# Case Study of Register-Transfer-Level (RTL) design Shift-Add Multiplier

Madhav Desai

March 20, 2017

#### Specification

- ▶ Input **start**, single bit, asserted by environment to indicate beginning of multiplication.
- Output done, single bit, asserted by system to indicate end of multiplication.
- ▶ Inputs **A**, **B**, each of 32-bit width, the two numbers to be multiplied.
- Output result, 32-bit product (bottom 32-bits of 64 bit true product).
- Inputs clock, reset: reset is active high, positive edge of clock is used.
- ▶ System computes the product of **A**, **B**.

#### RTL Algorithm

```
register AREG[31:0], BREG[31:0]
register PROD[63:0], TSUM[32:0], COUNT[5:0]
thread ShiftAddMul {
rst: if (start) then
       COUNT := 33, AREG := A, BREG := B, PROD := 0,
       goto decr
    else goto rst end if
 sumstate:
   COUNT := COUNT - 1,
   TSUM := (PROD[63:32] + (AREG[0] ? BREG : 0)),
   goto update
update:
   PROD := (TSUM && PROD[31:1]), AREG := (AREG >> 1)
   if(COUNT == 0) RESULT := PROD[31:0], goto done
   else goto sumstate
 donestate:
   done = 1, goto rst
```

#### The data-path: transfers

Use the following coding to mark the transfers:

```
T0
        COUNT := 33
Т1
        COUNT := COUNT - 1
T2
        AREG := A
Т3
        AREG := (AREG >> 1)
        BREG := B
T4
T5
        PROD := 0
Т6
        PROD := (0 \&\& TSUM \&\& PROD[32:1])
T7
        TSUM := (PROD[63:32] + (AREG[0]? B : 0)
        RESULT := PROD[31:0]
T8
```

#### The data-path: status signals

Use the following coding for the status predicates:

## The data-path: implement using muxes, combinational circuits, registers

 


Figure: Datapath for the counter

### The control-path: FSM

state	reset	start	S	next-state	T	TC	1T2	2T3	3T4	4T	5T6	3T	7T8	done
-	1	-	-	rst	-	-	-	-	-	-	-	-	-	-
rst	0	0	_	rst	0	0	0	0	0	0	0	0	0	0
rst	0	1	_	sumstate	1	0	1	0	1	1	0	0	0	0
sumstate	0	-	-	update	0	1	0	0	0	0	0	1	0	0
update	0	_	0	sumstate	0	0	0	1	0	0	1	0	0	0
update	0	_	1	donestate	0	0	0	1	0	0	1	0	1	0
donestate	e 0	_	_	rst	0	0	0	0	0	0	0	0	0	1

#### **VHDL**

- Entity/Architecture for Datapath.
- Entity/Architecture for Controlpath.
- Entity/Architecture for ShiftAddMultiplier.
- Component package: component declarations for ShiftAddMultiplier, Datapath, Controlpath.
- Entity/Architecture for Testbench.