

Lab Report : Arithmetic Logic Unit

Name : Saqib Azim

Roll No. : 150070031

Eight Bit Adder:

eightbitadder.vhd

```
library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

entity eightbitadder is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;

architecture behave of eightbitadder is
    component onebitadder is
        port(x,y,cin : in std_logic;
             z,cout : out std_logic);
    end component;
    signal c:std_logic_vector(7 downto 0);
begin
    adder0:onebitadder port map(x=>x(0),y=>y(0),cin=>'0',z=>z(0),cout=>c(0));
    adder1:onebitadder port map(x=>x(1),y=>y(1),cin=>c(0),z=>z(1),cout=>c(1));
    adder2:onebitadder port map(x=>x(2),y=>y(2),cin=>c(1),z=>z(2),cout=>c(2));
    adder3:onebitadder port map(x=>x(3),y=>y(3),cin=>c(2),z=>z(3),cout=>c(3));
    adder4:onebitadder port map(x=>x(4),y=>y(4),cin=>c(3),z=>z(4),cout=>c(4));
    adder5:onebitadder port map(x=>x(5),y=>y(5),cin=>c(4),z=>z(5),cout=>c(5));
    adder6:onebitadder port map(x=>x(6),y=>y(6),cin=>c(5),z=>z(6),cout=>c(6));
```

```

adder7:onebitadder port map(x=>x(7),y=>y(7),cin=>c(6),z=>z(7),cout=>c(7));
end behave;

```

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

```

```

entity onebitadder is
port (x,y,cin: in std_logic;
      z,cout:out std_logic);
end entity;


```

```


architecture behave of onebitadder is
begin
    z <= (cin xor (x xor y));
    cout <= ((cin and (x xor y)) or (x and y));
end behave;

```

Register Transfer Level Results-

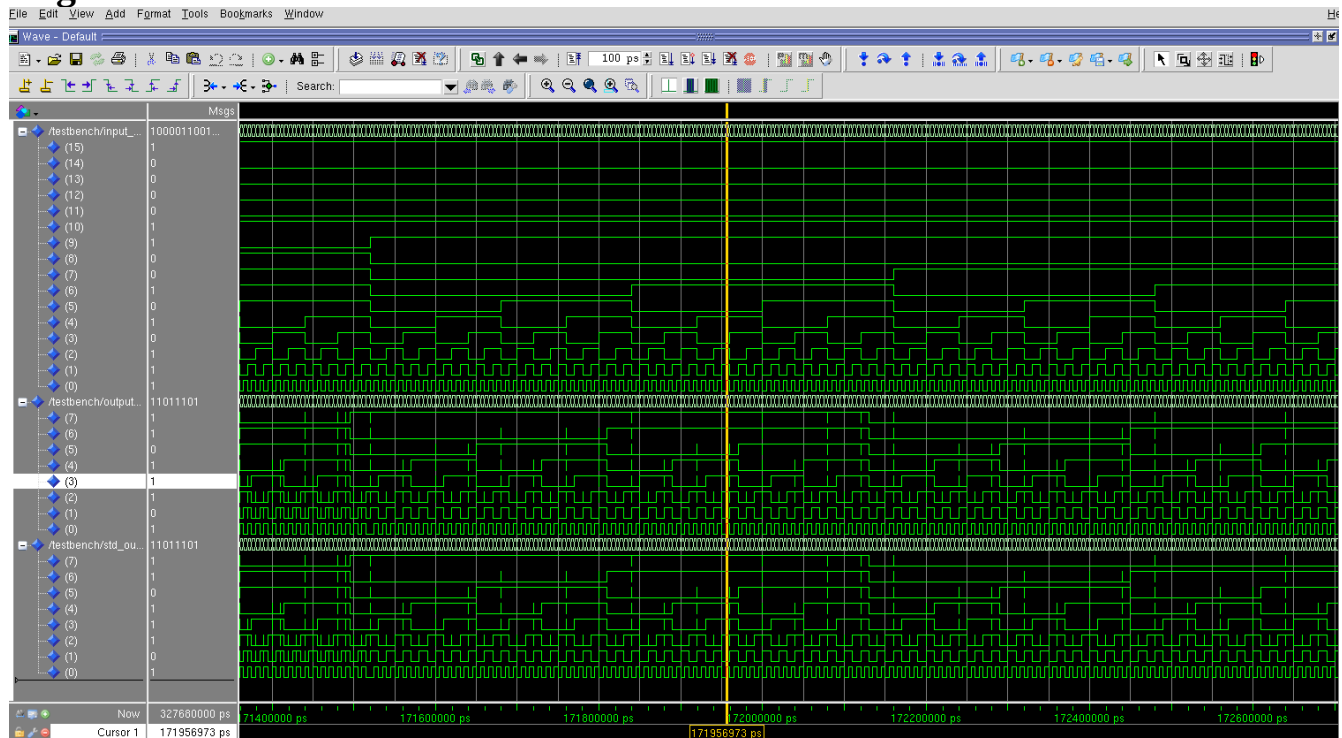

Gate Level Simulation

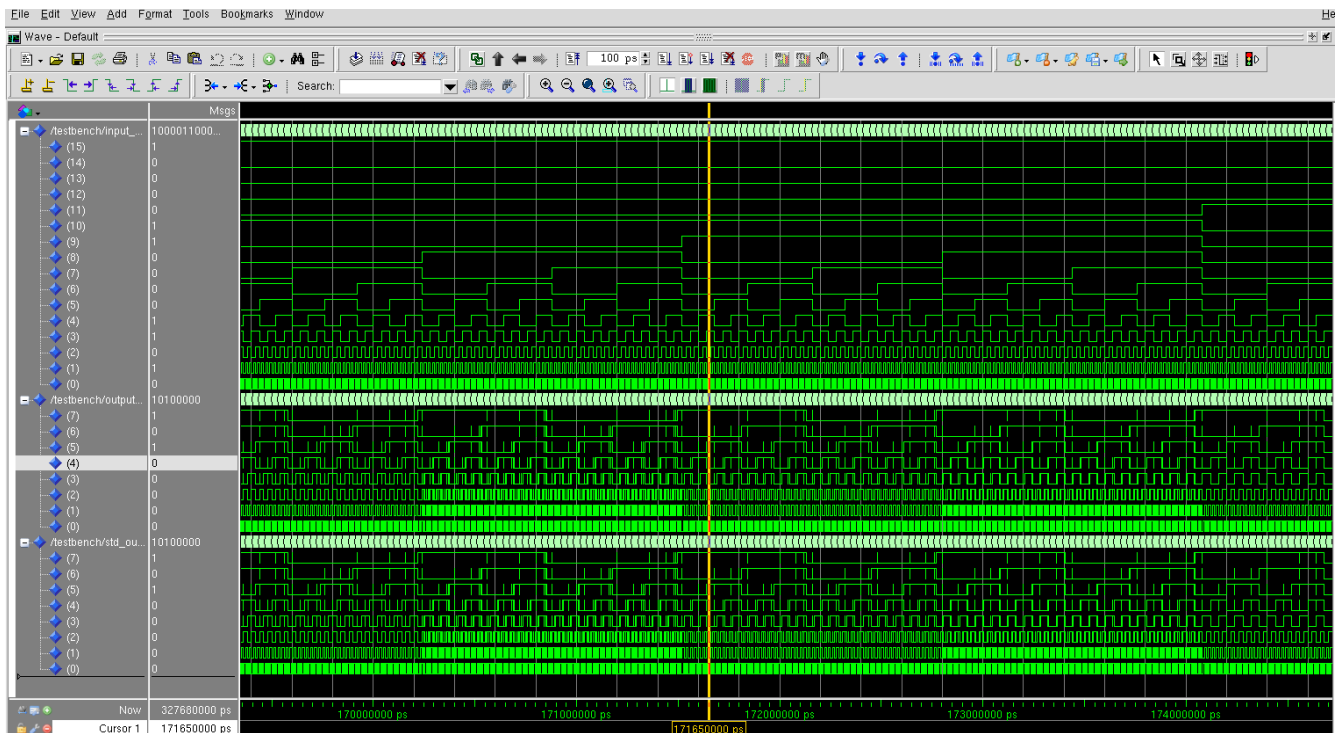

Eight Bit Subtractor:

eightbitsubtractor.vhd

```
library std;  
use std.standard.all;  
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity eightbitsubtractor is  
  port (x,y: in std_logic_vector(7 downto 0);  
        z:out std_logic_vector(7 downto 0));  
end entity;
```

```
architecture behave of eightbitsubtractor is  
  component onebitsubtractor is  
    port(x,y,cin : in std_logic;  
          z,cout : out std_logic);  
  end component;
```

```

    signal c:std_logic_vector(7 downto 0);
begin

    subtractor0:onebitsubtractor port
    map(x=>x(0),y=>y(0),cin=>'0',z=>z(0),cout=>c(0));
    subtractor1:onebitsubtractor port
    map(x=>x(1),y=>y(1),cin=>c(0),z=>z(1),cout=>c(1));
    subtractor2:onebitsubtractor port
    map(x=>x(2),y=>y(2),cin=>c(1),z=>z(2),cout=>c(2));
    subtractor3:onebitsubtractor port
    map(x=>x(3),y=>y(3),cin=>c(2),z=>z(3),cout=>c(3));
    subtractor4:onebitsubtractor port
    map(x=>x(4),y=>y(4),cin=>c(3),z=>z(4),cout=>c(4));
    subtractor5:onebitsubtractor port
    map(x=>x(5),y=>y(5),cin=>c(4),z=>z(5),cout=>c(5));
    subtractor6:onebitsubtractor port
    map(x=>x(6),y=>y(6),cin=>c(5),z=>z(6),cout=>c(6));
    subtractor7:onebitsubtractor port
    map(x=>x(7),y=>y(7),cin=>c(6),z=>z(7),cout=>c(7));
end behave;

```

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

```

```

entity onebitsubtractor is
port (x,y,cin: in std_logic;
      z,cout:out std_logic);
end entity;


```

```


architecture behave of onebitsubtractor is
begin
    z <= (cin xor (x xor y));
    cout <= ((not x) and cin) or ((not x) and y) or (cin and y);
end behave;

```

Register Transfer Level Results-

 

Gate Level Simulation Results-

 

Left Shifter:

leftshift.vhd

```
library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

entity leftshift is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;

architecture behave of leftshift is
    signal a, b:std_logic_vector(7 downto 0);
    signal c:std_logic;
begin
    c <= (not (y(7) or y(6) or y(5) or y(4) or y(3)));

    a(7) <= (x(3) and y(2)) or ((not y(2)) and x(7));
    a(6) <= (x(2) and y(2)) or ((not y(2)) and x(6));
    a(5) <= (x(1) and y(2)) or ((not y(2)) and x(5));
    a(4) <= (x(0) and y(2)) or ((not y(2)) and x(4));
    a(3) <= ((not y(2)) and x(3));
    a(2) <= ((not y(2)) and x(2));
    a(1) <= ((not y(2)) and x(1));
    a(0) <= ((not y(2)) and x(0));

    b(7) <= (a(5) and y(1)) or ((not y(1)) and a(7));
    b(6) <= (a(4) and y(1)) or ((not y(1)) and a(6));
    b(5) <= (a(3) and y(1)) or ((not y(1)) and a(5));
    b(4) <= (a(2) and y(1)) or ((not y(1)) and a(4));
    b(3) <= (a(1) and y(1)) or ((not y(1)) and a(3));
    b(2) <= (a(0) and y(1)) or ((not y(1)) and a(2));
    b(1) <= ((not y(1)) and a(1));
    b(0) <= ((not y(1)) and a(0));
```


```

z(7) <= ((b(6) and y(0)) or ((not y(0)) and b(7))) and c;
z(6) <= ((b(5) and y(0)) or ((not y(0)) and b(6))) and c;
z(5) <= ((b(4) and y(0)) or ((not y(0)) and b(5))) and c;
z(4) <= ((b(3) and y(0)) or ((not y(0)) and b(4))) and c;
z(3) <= ((b(2) and y(0)) or ((not y(0)) and b(3))) and c;
z(2) <= ((b(1) and y(0)) or ((not y(0)) and b(2))) and c;
z(1) <= ((b(0) and y(0)) or ((not y(0)) and b(1))) and c;
z(0) <= (((not y(0)) and b(0))) and c;


```

end behave;

Register Transfer Level Results-

 

Gate Level Simulation Results-

 

RightShifter:

rightshift.vhd

```
library std;  
use std.standard.all;  
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity rightshift is  
port (x,y: in std_logic_vector(7 downto 0);  
      z:out std_logic_vector(7 downto 0));  
end entity;
```

```
architecture behave of rightshift is  
    signal a, b:std_logic_vector(7 downto 0);  
    signal c:std_logic;
```


begin

c <= (not (y(7) or y(6) or y(5) or y(4) or y(3)));

a(0) <= (x(4) and y(2)) or ((not y(2)) and x(0));

a(1) <= (x(5) and y(2)) or ((not y(2)) and x(1));

a(2) <= (x(6) and y(2)) or ((not y(2)) and x(2));

a(3) <= (x(7) and y(2)) or ((not y(2)) and x(3));

a(4) <= ((not y(2)) and x(4));

a(5) <= ((not y(2)) and x(5));

a(6) <= ((not y(2)) and x(6));

a(7) <= ((not y(2)) and x(7));

b(0) <= (a(2) and y(1)) or ((not y(1)) and a(0));

b(1) <= (a(3) and y(1)) or ((not y(1)) and a(1));

b(2) <= (a(4) and y(1)) or ((not y(1)) and a(2));

b(3) <= (a(5) and y(1)) or ((not y(1)) and a(3));

b(4) <= (a(6) and y(1)) or ((not y(1)) and a(4));

b(5) <= (a(7) and y(1)) or ((not y(1)) and a(5));

b(6) <= ((not y(1)) and a(6));

b(7) <= ((not y(1)) and a(7));

z(0) <= ((b(1) and y(0)) or ((not y(0)) and b(0))) and c;

z(1) <= ((b(2) and y(0)) or ((not y(0)) and b(1))) and c;

z(2) <= ((b(3) and y(0)) or ((not y(0)) and b(2))) and c;

z(3) <= ((b(4) and y(0)) or ((not y(0)) and b(3))) and c;

z(4) <= ((b(5) and y(0)) or ((not y(0)) and b(4))) and c;


z(5) <= ((b(6) and y(0)) or ((not y(0)) and b(5))) and c;

z(6) <= ((b(7) and y(0)) or ((not y(0)) and b(6))) and c;


z(7) <= (((not y(0)) and b(7))) and c;

end behave;

Register Transfer Level Results-

 

Gate Level Simulation Results-

 

Arithmetic Logic Unit:

alu.vhd

```
-----  
library std;  
use std.standard.all;  
  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity alu is  
    port( X,Y : in std_logic_vector(7 downto 0); x0,x1 : in std_logic ; Z : out  
std_logic_vector(7 downto 0));  
end entity;  
  
architecture behave of alu is  
    signal sig1,sig2,sig3,sig4 : std_logic_vector(7 downto 0);  
  
    component eightbitadder is  
        port(x,y:in std_logic_vector(7 downto 0); z:out std_logic_vector(7  
downto 0));  
    end component;  
    --- Add component of eightbitsubtractor  
  
    component leftshift is  
        port( x,y : in std_logic_vector(7 downto 0);  
        z: out std_logic_vector(7 downto 0));  
    end component;  
    --- Add component of rightshift  
    component rightshift is  
        port( x,y : in std_logic_vector(7 downto 0);  
        z: out std_logic_vector(7 downto 0));  
    end component;  
  
    component eightbitsubtractor is
```

```

        port(x,y:in std_logic_vector(7 downto 0); z:out std_logic_vector(7
downto 0));
    end component;

```

```

-----
begin
a: eightbitadder    port map(x => X, y => Y, z => sig1);
b: leftshift        port map(x => X, y => Y, z => sig4);
c: rightshift       port map(x => X, y => Y, z => sig3);
d: eightbitsubtractor port map(x => X, y => Y, z => sig2);
-----

```

```

process(x0, x1,sig1, sig2, sig3, sig4)
begin

```

```

-----
if (x0 = '0' and x1 = '0') then
z<= sig1;
elsif(x0 = '1') and (x1 = '0') then
z<= sig2;
elsif(x0 = '0') and (x1 = '1') then
z<= sig3;
else
z<= sig4;
end if;
-----

```

```

end process;

```

```

end behave;

```

```

-----Eight Bit Adder-----

```

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

```

```

entity eightbitadder is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;

```

architecture behave of eightbitadder is

component onebitadder is

port(x,y,cin : in std_logic;

z,cout : out std_logic);

end component;

signal c:std_logic_vector(7 downto 0);

begin

adder0:onebitadder port map(x=>x(0),y=>y(0),cin=>'0',z=>z(0),cout=>c(0));

adder1:onebitadder port map(x=>x(1),y=>y(1),cin=>c(0),z=>z(1),cout=>c(1));

adder2:onebitadder port map(x=>x(2),y=>y(2),cin=>c(1),z=>z(2),cout=>c(2));

adder3:onebitadder port map(x=>x(3),y=>y(3),cin=>c(2),z=>z(3),cout=>c(3));

adder4:onebitadder port map(x=>x(4),y=>y(4),cin=>c(3),z=>z(4),cout=>c(4));

adder5:onebitadder port map(x=>x(5),y=>y(5),cin=>c(4),z=>z(5),cout=>c(5));

adder6:onebitadder port map(x=>x(6),y=>y(6),cin=>c(5),z=>z(6),cout=>c(6));

adder7:onebitadder port map(x=>x(7),y=>y(7),cin=>c(6),z=>z(7),cout=>c(7));

end behave;

library std;

use std.standard.all;

library ieee;

use ieee.std_logic_1164.all;

entity onebitadder is

port (x,y,cin: in std_logic;

z,cout:out std_logic);

end entity;

architecture behave of onebitadder is

begin

z <= (cin xor (x xor y));

cout <= ((cin and (x xor y)) or (x and y));

end behave;

-----Left Shifter-----

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

entity leftshift is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;

architecture behave of leftshift is
    signal a, b:std_logic_vector(7 downto 0);
    signal c:std_logic;
begin
    c <= (not (y(7) or y(6) or y(5) or y(4) or y(3)));

    a(7) <= (x(3) and y(2)) or ((not y(2)) and x(7));
    a(6) <= (x(2) and y(2)) or ((not y(2)) and x(6));
    a(5) <= (x(1) and y(2)) or ((not y(2)) and x(5));
    a(4) <= (x(0) and y(2)) or ((not y(2)) and x(4));
    a(3) <= ((not y(2)) and x(3));
    a(2) <= ((not y(2)) and x(2));
    a(1) <= ((not y(2)) and x(1));
    a(0) <= ((not y(2)) and x(0));

    b(7) <= (a(5) and y(1)) or ((not y(1)) and a(7));
    b(6) <= (a(4) and y(1)) or ((not y(1)) and a(6));
    b(5) <= (a(3) and y(1)) or ((not y(1)) and a(5));
    b(4) <= (a(2) and y(1)) or ((not y(1)) and a(4));
    b(3) <= (a(1) and y(1)) or ((not y(1)) and a(3));
    b(2) <= (a(0) and y(1)) or ((not y(1)) and a(2));
    b(1) <= ((not y(1)) and a(1));
    b(0) <= ((not y(1)) and a(0));

    z(7) <= ((b(6) and y(0)) or ((not y(0)) and b(7))) and c;
    z(6) <= ((b(5) and y(0)) or ((not y(0)) and b(6))) and c;
    z(5) <= ((b(4) and y(0)) or ((not y(0)) and b(5))) and c;
    z(4) <= ((b(3) and y(0)) or ((not y(0)) and b(4))) and c;
    z(3) <= ((b(2) and y(0)) or ((not y(0)) and b(3))) and c;

```

```

z(2) <= ((b(1) and y(0)) or ((not y(0)) and b(2))) and c;
z(1) <= ((b(0) and y(0)) or ((not y(0)) and b(1))) and c;
z(0) <= (((not y(0)) and b(0))) and c;

```

```

end behave;

```

```

-----
-----Right Shifter-----

```

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

```

```

entity rightshift is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;

```

```

architecture behave of rightshift is
    signal a, b:std_logic_vector(7 downto 0);
    signal c:std_logic;
begin
c <= (not (y(7) or y(6) or y(5) or y(4) or y(3)));

```

```

a(0) <= (x(4) and y(2)) or ((not y(2)) and x(0));
a(1) <= (x(5) and y(2)) or ((not y(2)) and x(1));
a(2) <= (x(6) and y(2)) or ((not y(2)) and x(2));
a(3) <= (x(7) and y(2)) or ((not y(2)) and x(3));
a(4) <= ((not y(2)) and x(4));
a(5) <= ((not y(2)) and x(5));
a(6) <= ((not y(2)) and x(6));
a(7) <= ((not y(2)) and x(7));

```

```

b(0) <= (a(2) and y(1)) or ((not y(1)) and a(0));
b(1) <= (a(3) and y(1)) or ((not y(1)) and a(1));
b(2) <= (a(4) and y(1)) or ((not y(1)) and a(2));
b(3) <= (a(5) and y(1)) or ((not y(1)) and a(3));
b(4) <= (a(6) and y(1)) or ((not y(1)) and a(4));

```

```
b(5) <= (a(7) and y(1)) or ((not y(1)) and a(5));
b(6) <= ((not y(1)) and a(6));
b(7) <= ((not y(1)) and a(7));
```

```
z(0) <= ((b(1) and y(0)) or ((not y(0)) and b(0))) and c;
z(1) <= ((b(2) and y(0)) or ((not y(0)) and b(1))) and c;
z(2) <= ((b(3) and y(0)) or ((not y(0)) and b(2))) and c;
z(3) <= ((b(4) and y(0)) or ((not y(0)) and b(3))) and c;
z(4) <= ((b(5) and y(0)) or ((not y(0)) and b(4))) and c;
z(5) <= ((b(6) and y(0)) or ((not y(0)) and b(5))) and c;
z(6) <= ((b(7) and y(0)) or ((not y(0)) and b(6))) and c;
z(7) <= (((not y(0)) and b(7))) and c;
```

```
end behave;
```

-----Eight Bit Subtractor-----

```
library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;
```

```
entity eightbitsubtractor is
port (x,y: in std_logic_vector(7 downto 0);
      z:out std_logic_vector(7 downto 0));
end entity;
```

```
architecture behave of eightbitsubtractor is
    component onebitsubtractor is
        port(x,y,cin : in std_logic;
              z,cout : out std_logic);
    end component;
    signal c:std_logic_vector(7 downto 0);
begin
```

```
    subtractor0:onebitsubtractor port
map(x=>x(0),y=>y(0),cin=>'0',z=>z(0),cout=>c(0));
```



```

    subtractor1:onebitsubtractor port
map(x=>x(1),y=>y(1),cin=>c(0),z=>z(1),cout=>c(1));
    subtractor2:onebitsubtractor port
map(x=>x(2),y=>y(2),cin=>c(1),z=>z(2),cout=>c(2));
    subtractor3:onebitsubtractor port
map(x=>x(3),y=>y(3),cin=>c(2),z=>z(3),cout=>c(3));
    subtractor4:onebitsubtractor port
map(x=>x(4),y=>y(4),cin=>c(3),z=>z(4),cout=>c(4));
    subtractor5:onebitsubtractor port
map(x=>x(5),y=>y(5),cin=>c(4),z=>z(5),cout=>c(5));
    subtractor6:onebitsubtractor port
map(x=>x(6),y=>y(6),cin=>c(5),z=>z(6),cout=>c(6));
    subtractor7:onebitsubtractor port
map(x=>x(7),y=>y(7),cin=>c(6),z=>z(7),cout=>c(7));
end behave;

```

```

library std;
use std.standard.all;
library ieee;
use ieee.std_logic_1164.all;

```

```

entity onebitsubtractor is
port (x,y,cin: in std_logic;
      z,cout:out std_logic);
end entity;

```

```

architecture behave of onebitsubtractor is
begin
    z <= (cin xor (x xor y));
    cout <= ((not x) and cin) or ((not x) and y) or (cin and y);
end behave;

```

Testbench.vhd

```

library std;
use std.textio.all;

```

```
library std;
use std.standard.all;
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity Testbench is
end entity;
architecture Behave of Testbench is
```

```
-----
-- edit the following lines to set the number of i/o's of your
-- DUT.
```

```
-----
constant number_of_inputs : integer := 18; -- # input bits to your design.
constant number_of_outputs : integer := 8; -- # output bits from your design.
```

```
-- component port widths..
component DUT is
  port(input_vector: in std_logic_vector(number_of_inputs-1 downto 0);
        output_vector: out std_logic_vector(number_of_outputs-1 downto 0));
end component;
```

```
-- end editing.
```

```
-----
-----
signal input_vector : bit_vector(number_of_inputs-1 downto 0);
signal output_vector : bit_vector(number_of_outputs-1 downto 0);
signal std_output_vector : std_logic_vector(number_of_outputs-1 downto 0);
```

```
-- create a constrained string outof
function to_string(x: string) return string is
  variable ret_val: string(1 to x'length);
  alias lx : string (1 to x'length) is x;
begin
  ret_val := lx;
  return(ret_val);
```

```
end to_string;
```

```
begin
```

```
  process
```

```
    variable err_flag : boolean := false;
```

```
    File INFILE: text open read_mode is
```

```
"/home/saqib1707/Acads/4thsem/EE214_Digital_Circuits_Lab/ALU/ALU_exp/src/alu_TRACEFILE.txt";
```

```
    FILE OUTFILE: text open write_mode is
```

```
"/home/saqib1707/Acads/4thsem/EE214_Digital_Circuits_Lab/ALU/ALU_exp/src/OUTPUTS.txt";
```

```
-----  
-- edit the next two lines to customize  
-----
```

```
variable input_vector_var: bit_vector (number_of_inputs-1 downto 0);
```

```
variable output_vector_var: bit_vector (number_of_outputs-1 downto 0);
```

```
variable output_mask_var: bit_vector (number_of_outputs-1 downto 0);
```

```
variable output_comp_var: bit_vector (number_of_outputs-1 downto 0);
```

```
constant ZZZZ : bit_vector(number_of_outputs-1 downto 0) := (others => '0');  
-----
```

```
variable INPUT_LINE: Line;
```

```
variable OUTPUT_LINE: Line;
```

```
variable LINE_COUNT: integer := 0;
```

```
begin
```

```
  while not endfile(INFILE) loop
```

```
    -- will read a new line every 5ns, apply input,
```

```
    -- wait for 1 ns for circuit to settle.
```

```
    -- read output.
```

```
    LINE_COUNT := LINE_COUNT + 1;
```

```
    -- read input at current time.
```

```
    readLine (INFILE, INPUT_LINE);
```

```

read (INPUT_LINE, input_vector_var);
read (INPUT_LINE, output_vector_var);
read (INPUT_LINE, output_mask_var);

-- apply input.
input_vector <= input_vector_var;

-- wait for the circuit to settle
wait for 1 ns;

-- check output.
output_comp_var := (output_mask_var and (output_vector xor
output_vector_var));
if (output_comp_var /= ZZZZ) then
  write(OUTPUT_LINE,to_string("ERROR: line "));
  write(OUTPUT_LINE, LINE_COUNT);
  writeline(OUTFILE, OUTPUT_LINE);
  err_flag := true;
end if;

write(OUTPUT_LINE, input_vector);
write(OUTPUT_LINE, to_string(" "));
write(OUTPUT_LINE, output_vector);
writeline(OUTFILE, OUTPUT_LINE);

-- advance time by 4 ns.
wait for 4 ns;
end loop;

assert (err_flag) report "SUCCESS, all tests passed." severity note;
assert (not err_flag) report "FAILURE, some tests failed." severity error;

wait;
end process;

output_vector <= to_bitvector(std_output_vector);
dut_instance: DUT
  port map(input_vector => to_stdlogicvector(input_vector), output_vector
=>std_output_vector );

```

```
end Behave;
```

DUT.vhd

```
-- A DUT entity is used to wrap your design.  
-- This example shows how you can do this for the  
-- eight-bit adder.
```

```
library std;  
use std.standard.all;
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity DUT is
```

```
    port(input_vector: in std_logic_vector(17 downto 0); ---Note: for alu testing (17  
downto 0) for others (15 downto 0)
```

```
        output_vector: out std_logic_vector(7 downto 0));  
end entity;
```

```
architecture DutWrap of DUT is
```

```
    --- Add component of eightbitadder  
    --- Add component of eightbitsubtractor  
    --- Add component of leftshift  
    --- Add component of rightshift
```

```
    component alu is
```

```
        port( X,Y : in std_logic_vector(7 downto 0); x0,x1 : in std_logic ; Z : out  
std_logic_vector(7 downto 0));  
    end component;
```

```
begin
```


```
    -- input/output vector element ordering is critical,  
    -- and must match the ordering in the trace file!
```

```
--a: eightbitadder port map(x => input_vector(15 downto 8), y =>input_vector(7  
downto 0) , z=> output_vector);
```

```
--b: leftshift          port map(x => input_vector(15 downto 8), y  
=>input_vector(7 downto 0) , z=> output_vector);
```

```
--c: rightshift      port map(x => input_vector(15 downto 8), y =>input_vector(7
downto 0) , z=> output_vector);
--d: eightbitsubtractor port map(x => input_vector(15 downto 8), y
=>input_vector(7 downto 0) , z=> output_vector); --- Note: z = x- y
add_instance: alu port map( X => input_vector(15 downto 8), Y => input_vector(7
downto 0) , x0 => input_vector(16) , x1 => input_vector(17), Z => output_vector);
end DutWrap;
```

Register Transfer Level Results-

 

Gate Level Simulation Results-

